

# O P JINDAL SCHOOL, SAVITRINAGAR

## CLASS NOTES


CLASS XII PHYSICS

Date : 29 /04/20

TOPIC : CURRENT ELECTRICITY

SUBTOPIC: POTENTIOMETER

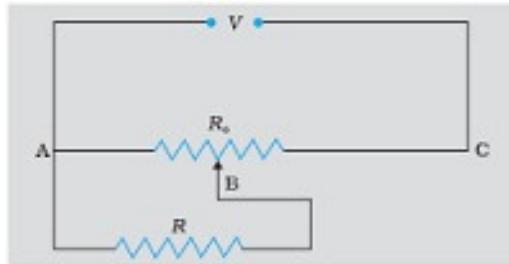**Problem:-** A resistance of  $R \Omega$  draws current from a potentiometer. The potentiometer has a total resistance  $R_0 \Omega$ (Fig.). A voltage  $V$  is supplied to the potentiometer. Derive an expression for the voltage across  $R$  when the sliding contact is in the middle of the potentiometer.



**Answer:** - While the slide is in the middle of the potentiometer only half of its resistance ( $R_0/2$ ) will be between the points A and B. Hence, the total resistance between A and B, say,  $R_1$ , will be given by the following expression:

$$(1/R_1) = (1/R) + (1/R_0/2)$$

$$R_1 = (R_0 R) / (R_0 + 2R)$$

The total resistance between A and C will be sum of resistance between A and B and B and C, i.e.,  $(R_1 + R_0/2)$

∴ The current flowing through the potentiometer will be

$$I = (V) / (R_1 + R_0/2)$$

The voltage  $V_1$  taken from the potentiometer will be the product of current I and resistance  $R_1$ ,

$$V_1 = I R_1 = (2V) / (2R_1 R_0) \times R_1$$

Substituting for  $R_1$ , we have a

$$V_1 = (2V) / ((2(R_0 \times R) / (R_0 + 2R)) + R_0) \times ((R_0 \times R) / (R_0 + 2R))$$

$$V_1 = (2VR) / (2R + R_0 + 2R)$$

$$\text{Or } V_1 = (2VR) / (R_0 + 4R)$$

**Problem:-** In a potentiometer arrangement, a cell of Emf 1.25V gives a balance point at 35.0 cm length of the wire. If a cell is replaced by another cell and the balance point shifts to 63.0 cm, what is the Emf of the second cell?

**Answer:-** Emf of the cell,  $E_1=1.25V$

Balance point of the potentiometer,  $I_1=35\text{cm}$

The cell is replaced by another cell of Emf  $E_2$ .

New balance point of the potentiometer,  $I_2=63\text{cm}$

The balance condition id given by the relation,

$$(E_1/E_2) = (I_1/I_2)$$


$$E_2 = E_1 \times (I_2/I_1)$$

$$= 1.25 \times (63/35)$$

$$= 2.25V.$$

Therefore, Emf of the second cell is 2.25 V.

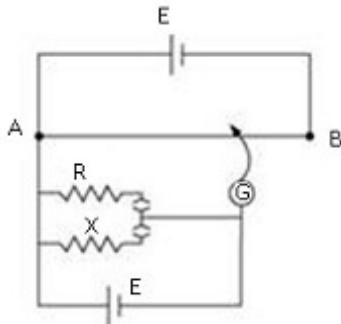**Problem:-** Figure shows a potentiometer circuit for comparison of two resistances. The balance point with a standard resistor  $R = 10.0$  is found to be 58.3 cm, while that with the unknown resistance  $X$  is 68.5 cm. Determine the value of  $X$ . What might you do if you failed to find a balance point with the given cell of Emf?



**Answer:-**

Resistance of the standard resistor,  $R = 10.0$

Balance point for this resistance,  $I_1 = 58.3$  cm

Current in the potentiometer wire =  $i$

Hence, potential drop across  $R$ ,  $E_1 = iR$

Resistance of the unknown resistor =  $X$

Balance point for this resistor,  $I_2 = 68.5$  cm

Hence, potential drop across  $X$ ,  $E_2 = iX$

The relation connecting Emf and balance point is,

$$(E_1 / E_2) = (I_1 / I_2)$$

$$(iR) / (iX) = (I_1 / I_2)$$

$$X = (I_1 / I_2) \times R$$

$$= (68.5 / 58.3) \times 10$$

$$= 11.749\Omega$$

Therefore, the value of the unknown resistance,  $X$ , is  $11.75\Omega$ .

If we fail to find a balance point with the given cell of Emf,  $E$ , then the potential drop across  $R$  and  $X$  must be reduced by putting a resistance in series with it. Only if the potential drop across  $R$  or  $X$  is smaller than the potential drop across the potentiometer wire  $AB$ , a balance point is obtained.