

O P JINDAL SCHOOL, SAVITRINAGAR

PRACTICE PAPER-10

CLASS XII PHYSICS


TOPIC : CURRENT ELECTRICITY

Date : 08/05/20


- Q1 Why are the connections between resistors in a Wheatstone or meter bridge made of thick copper strips.
- Q2 Why manganin wire is used for making wire of meter bridge or potentiometer.
- Q3 Write the factors on which the sensitivity of Wheatstone bridge depends. Write the conditions for most sensitive.

- Q4 Write the principle on which (statements)
- meter bridge works
 - Potentiometer works

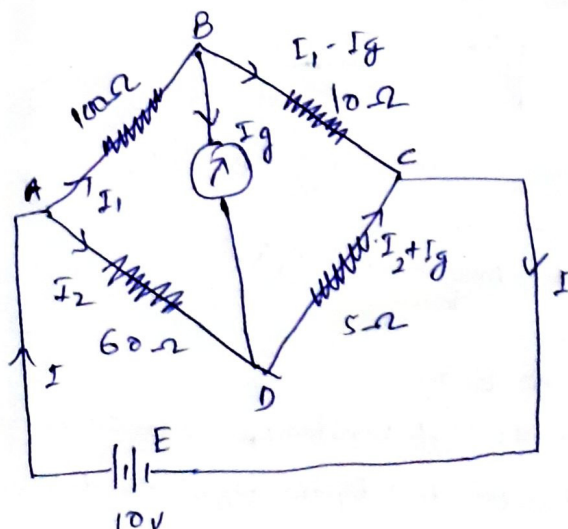- Q5 The four arms of a Wheatstone bridge have following resistance $AB = 100\Omega$, $BC = 10\Omega$, $CD = 5\Omega$ and $DA = 60\Omega$ find the current in each branch of circuit.




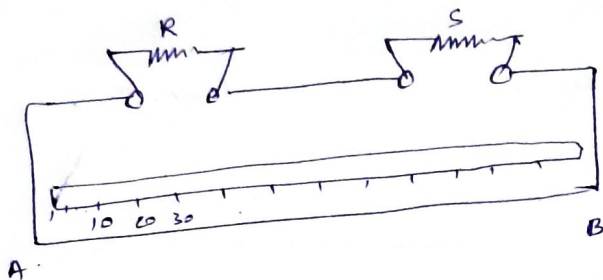- Q6 In a meter bridge the null point is found at a distance of 33.7 cm from A. If now a resistance of 12Ω is connected in parallel with S, the null point occurs at 51.9 cm. Determine the values of P and S.



Q 7 State the working principle of potentiometer, explain with help of circuit diagram how the potentiometer is using to compare the emf of two primary cell.

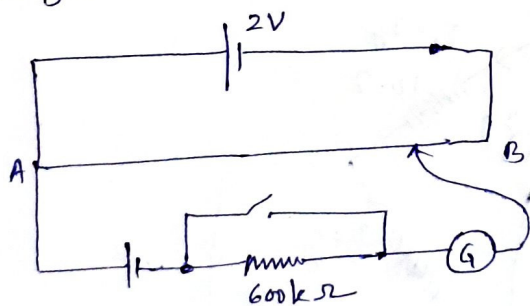Q 8 Figure shows a potentiometer with a cell of 2V and internal resistance 0.4Ω maintaining a potential drop across the resistor with wire AB. A standard cell which maintains a constant emf of 1.02V gives a balance point at 67.3 cm length of the wire. To ensure very low currents drawn from the standard cell a very high resistance of $600k\Omega$ is put in series with it, which is shunted closed to the balance point. The standard cell is then replaced by a cell of unknown emf E and the balance point found similarly turns out to be at 82.3 cm length of the wire.



- Q1 What is the value of E ?
- Q2 What purpose does the high resistance of $600k\Omega$ have?
- Q3 Is the balance point affected by the high resistance?
- Q4 Is the balance point affected by the internal resistance of driver cell?
- Q5 Would the method work in the above situation if the driver cell of the potentiometer had an emf of 1V instead of 2V?
- Q6 Would the circuit work well for determining an extremely small emf, say of the order of a few mV?

