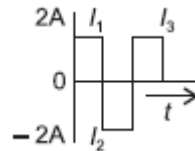


**O P JINDAL SCHOOL, SAVITRINAGAR**


**ASSIGNMENT**

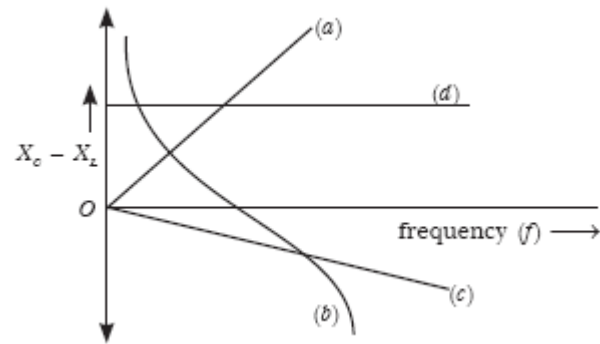**CLASS XII PHYSICS**

- 
- 1 Why is the use of ac voltage preferred over dc voltage? 1
  - 2 The peak value of emf in ac is  $E_0$ . Write its (i) rms, and (ii) average value over a complete cycle. 1
  - 3 The current flowing through a pure inductor of inductance 4mH is  $i = 12 \cos 300 t$  ampere. What is (i) rms, and (ii) average value of the current for a complete cycle? 1
  - 4 Calculate the rms value of the alternating current shown in the figure. 1



- 5 In a series  $LCR$  circuit, the voltages across an inductor, a capacitor and a resistor are 30 V, 30V and 60V respectively. What is the phase difference between the applied voltage and the current in the circuit? 1
- 6 Can a capacitor of suitable capacitance replace a inductor coil in an  $AC$  circuit? 1
- 7 When an alternating current is passed through a moving coil galvanometer, it shows no deflection. Why? 1
- 8 Which of the following curves may represent the reactance of a series  $LC$  combination? 1



- 9 In a series  $LCR$  circuit,  $V_L = V_C \neq V_R$ . What is the value of power factor? 1
- 10 The power factor of an ac circuit is 0.5. What is the phase difference between voltage and current in this circuit? 1